

Lab 6 - Datapath for I,J,R type

CECS 341 - Computer Architecture Organization

Student Antonio Ojeda SID 026076048

Student Bridget Naylor SID 025531413

Professor: Jose Aceves



California State University, Long Beach

College of Engineering
1250 Bellflower Blvd, Long Beach, CA 90840
Lab 2/12/2021

Lab 6-I-Type

CECS 341 Spring 2021

Goal/Objective:

Our goal is to modify our existing lab to make it able to execute jump instructions.

Technical Description/Steps:(include screenshots and description here)

To make the existing program execute jump instructions, we needed another mux and a shift left. We also needed to add a jump variable to our ALU to switch depending on the instruction.

```
wire branchSrc,  
wire jump;  
wire [31:0] SignExtend;  
  
//Output wires for mux  
wire [4:0] RegDstMux;  
wire [31:0] MemtoRegMux;  
wire [31:0] ALUSrcMux;  
wire [31:0] BranchSrcMux;  
wire [31:0] JumpMux;  
  
//Create logic for muxes  
assign RegDstMux = (RegDst == 1) ? instructionMemOutputWire[15:11] : instructionMemOutputWire[20:16];  
assign MemtoRegMux = (MemtoReg == 1) ? DataMemOut : ALUOutputWire;  
assign ALUSrcMux = (ALUSrc == 1) ? SignExtend : rtRTOOutputWire;  
assign BranchSrcMux = (Branchsrc == 1) ? pcaOutputWire1 : pcaOutputWire;  
assign JumpMux = (jump == 1) ? {pcaOutputWire[31:28], instructionMemOutputWire[25:0], 2'b00} : BranchSrcMux;
```

This image includes the addition of the jump wire, as well as the JumpMux wire and the assignment of JumpMux between the new jump address and the output of the branch mux. The new jump address is a concatenation of the bits [31:28] of the first PC adder output, bits [25:0] of the instruction, and 2 additional bits as a result of shifting left 2 times.

```

control ctrl(.Op(instructionMemOutputWire[31:26]),
             .Func(instructionMemOutputWire[5:0]),
             .RegWrite(controlRegRWriteOutputWire),
             .ALUCtrl(controlALUCntlOutputWire),
             .RegDst(RegDst),
             .Branch(Branch),
             .MemRead(MemRead),
             .MemWrite(MemWrite),
             .MemtoReg(MemtoReg),
             .ALUsrc(ALUsrc),
             .jump(jump));

```

The last connection port of ctrl is connected to the jump wire.

```

PC pcr(.clock(clk),
       .Reset(reset),
       .Din(JumpMux),
       .PC_out(pcrOutputWire));

```

This PC register has an additional port where instead of the output of the branch mux going into it, the output of the jump mux contains the new instruction address.

```

6'h02: begin    //j
    ALUCtrl = 4'b0;
    RegWrite = 1'b0;
    RegDst = 1'b0;
    Branch = 2'b0;
    MemRead = 1'b0;
    MemWrite = 1'b0;
    MemtoReg = 1'b0;
    ALUsrc = 1'b0;
    jump = 1'b1;
end

```

This new jump control case outputs signals to no other output signals except for jump.

```
|00 00 08 20
00 00 09 20
05 00 0A 34
00 00 0B 20
2A 60 0A 01
05 00 80 11
00 00 6C 8D
20 48 2C 01
01 00 08 21
04 00 6B 21
04 00 00 08
00 00 68 AD
04 00 69 AD
08 00 6A AD
0C 00 6B AD
```

This is the instruction memory file we translated from the MIPS instructions. It is set in the Little Endian format.

The following images are unchanged except for the relating to the jump modification.

Datapath:

```

module Datapath(
    input clk,
    input reset,
    output [31:0] Dout
);

    wire [31:0] pcaOutputWire;
    wire [31:0] pcaOutputWire1;
    wire [31:0] pcrOutputWire;
    wire [31:0] rfrsOutputWire;
    wire [31:0] rtRTOutputWire;
    wire [31:0] instructionMemOutputWire;
    wire controlRegRWriteOutputWire;
    wire [3:0] controlALUCnt1OutputWire;
    wire [31:0] ALUOutputWire;
    wire [31:0] DataMemOut;
    wire N;
    wire Z;
    wire C;
    wire V;
    wire RegDst;
    wire MemWrite;
    wire MemRead;
    wire [1:0] Branch;
    wire MemtoReg;
    wire ALUsrc;
    wire Branchsrc;
    wire jump;
    wire [31:0] SignExtend;

    //Output wires for mux
    wire [4:0] RegDstMux;
    wire [31:0] MemtoRegMux;
    wire [31:0] ALUsrcMux;
    wire [31:0] BranchSrcMux;
    wire [31:0] JumpMux;

    //Create logic for muxes
    assign RegDstMux = (RegDst == 1) ? instructionMemOutputWire[15:11] : instructionMemOutputWire[20:16];
    assign MemtoRegMux = (MemtoReg == 1) ? DataMemOut : ALUOutputWire;
    assign ALUsrcMux = (ALUsrc == 1) ? SignExtend : rtRTOutputWire;
    assign BranchSrcMux = (Branchsrc == 1) ? pcaOutputWire1 : pcaOutputWire;
    assign JumpMux = (jump == 1) ? {pcaOutputWire[31:28], instructionMemOutputWire[25:0], 2'b00} : BranchSrcMux;

```

```

control ctrl(.Op(instructionMemOutputWire[31:26]),
             .Func(instructionMemOutputWire[5:0]),
             .RegWrite(controlRegRWriteOutputWire),
             .ALUCtrl(controlALUCntlOutputWire),
             .RegDst(RegDst),
             .Branch(Branch),
             .MemRead(MemRead),
             .MemWrite(MemWrite),
             .MemtoReg(MemtoReg),
             .ALUsrc(ALUsrc),
             .jump(jump));
Instruction_Memory im(.Addr(pcrOutputWire),
                    .Inst_out(instructionMemOutputWire));
regfile32 rf(.clk(clk),
            .reset(reset),
            .D_En(controlRegRWriteOutputWire),
            .D_Addr(RegDstMux),
            .S_Addr(instructionMemOutputWire[25:21]),
            .T_Addr(instructionMemOutputWire[20:16]),
            .D(MemtoRegMux),
            .S(rfRSOutputWire),
            .T(rtRTOutputWire));
PCADD pca(.Din(pcrOutputWire),
         .PCADD_out(pcaOutputWire));
PCADDl pcal(.PCADDIn(pcaOutputWire),
          .SignEx(SignExtend),
          .NextPC(pcaOutputWire1));
BranchSrc bsrc(.BranchIn(Branch),
              .Zero(Z),
              .BranchOut(Branchsrc));
PC pcr(.clock(clk),
     .Reset(reset),
     .Din(JumpMux),
     .PC_out(pcrOutputWire));
ALU alu(.A(rfRSOutputWire),
      .B(ALUsrcMux),
      .ALUCtrl(controlALUCntlOutputWire),
      .ALUout(ALUOutputWire),
      .N(N), .C(C), .Z(Z), .V(V));

DataMem dm(.clk(clk),
          .mem_wr(MemWrite),
          .mem_rd(MemRead),
          .addr(ALUOutputWire),
          .wr_data(rtRTOutputWire),
          .rd_data(DataMemOut));
SignExtension se(.SignExtIn(instructionMemOutputWire[15:0]),
                .SignExtOut(SignExtend));
assign Dout = MemtoRegMux;
endmodule

```

Control:

```
module control(
    input [5:0] Op,
    input [5:0] Func,
    output reg RegWrite,
    output reg [3:0] ALUCtrl,
    output reg RegDst,
    output reg [1:0] Branch,
    output reg MemRead,
    output reg MemWrite,
    output reg MemtoReg,
    output reg ALUsrc,
    output reg jump
);

always@(*) begin
    if (Op == 6'b0) begin        //Detects R-Type Instruction
        RegWrite = 1'b1;        //Writes back to register file
        RegDst = 1'b1;          //Inst[15:11] as write back address
        Branch = 2'b00;
        MemRead = 1'b0;
        MemWrite = 1'b0;
        MemtoReg = 1'b0;
        ALUsrc = 1'b0;
        jump = 1'b0;
        case(Func)
            6'h20: ALUCtrl = 4'b1010; //Add signed
            6'h21: ALUCtrl = 4'b0010; //Add unsigned
            6'h22: ALUCtrl = 4'b1110; //Subtract signed
            6'h23: ALUCtrl = 4'b0110; //Subtract unsigned
            6'h24: ALUCtrl = 4'b0000; //AND
            6'h25: ALUCtrl = 4'b0001; //OR
            6'h26: ALUCtrl = 4'b0011; //XOR
            6'h27: ALUCtrl = 4'b1100; //NOR
            6'h2a: ALUCtrl = 4'b1111; //Set less than signed
            6'h2b: ALUCtrl = 4'b0100; //Set less than unsigned
            default: ALUCtrl = 4'bxxxx; //default to AND
        endcase
    end
end
```

```

else begin
    case(Op)
        6'h08: begin //addi
            ALUCtrl = 4'b1010; //Add ALU content
            RegWrite = 1'b1; //Write back to register file
            RegDst = 1'b0; //Inst[20:16] write back address
            Branch = 2'b00; //No branch performed
            MemRead = 1'b0; //No read from data memory
            MemWrite = 1'b0; //No write to data memory
            MentoReg = 1'b0; //Write back data comes from ALU
            ALUsrc = 1'b1; //Source B comes from SE immediate
            jump = 1'b0;
        end
        6'h09: begin //addiu
            ALUCtrl = 4'b0010;
            RegWrite = 1'b1;
            RegDst = 1'b0;
            Branch = 2'b00;
            MemRead = 1'b0;
            MemWrite = 1'b0;
            MentoReg = 1'b0;
            ALUsrc = 1'b1;
            jump = 1'b0;
        end
        6'h0c: begin //andi
            ALUCtrl = 4'b0000;
            RegWrite = 1'b1;
            RegDst = 1'b0;
            Branch = 2'b00;
            MemRead = 1'b0;
            MemWrite = 1'b0;
            MentoReg = 1'b0;
            ALUsrc = 1'b1;
            jump = 1'b0;
        end
        6'h0d: begin //ori
            ALUCtrl = 4'b0001;
            RegWrite = 1'b1;
            RegDst = 1'b0;
            Branch = 2'b00;
            MemRead = 1'b0;
            MemWrite = 1'b0;
            MentoReg = 1'b0;
            ALUsrc = 1'b1;
            jump = 1'b0;
        end
    end
end

```



```

6'h23: begin    //lw
    ALUCtrl = 4'b0010;
    RegWrite = 1'b1;
    RegDst = 1'b0;
    Branch = 2'b00;
    MemRead = 1'b1;
    MemWrite = 1'b0;
    MemtoReg = 1'b1;
    ALUsrc = 1'b1;
    jump = 1'b0;
end
6'h2b: begin    //sw
    ALUCtrl = 4'b0010;
    RegWrite = 1'b0;
    RegDst = 1'b0;
    Branch = 2'b00;
    MemRead = 1'b0;
    MemWrite = 1'b1;
    MemtoReg = 1'b0;
    ALUsrc = 1'b1;
    jump = 1'b0;
end
6'h04: begin    //beq
    ALUCtrl = 4'b0110;
    RegWrite = 1'b0;
    RegDst = 1'b0;
    Branch = 2'b01;
    MemRead = 1'b0;
    MemWrite = 1'b0;
    MemtoReg = 1'b0;
    ALUsrc = 1'b0;
    jump = 1'b0;
end
6'h05: begin    //bnq
    ALUCtrl = 4'b0110;
    RegWrite = 1'b0;
    RegDst = 1'b0;
    Branch = 2'b10;
    MemRead = 1'b0;
    MemWrite = 1'b0;
    MemtoReg = 1'b0;
    ALUsrc = 1'b0;
    jump = 1'b0;
end
6'h0a: begin    //slti
    ALUCtrl = 4'b1111;
    RegWrite = 1'b1;
    RegDst = 1'b0;
    Branch = 2'b00;
    MemRead = 1'b0;
    MemWrite = 1'b0;
    MemtoReg = 1'b0;
    ALUsrc = 1'b1;
    jump = 1'b0;
end
6'h0b: begin    //sltiu
    ALUCtrl = 4'b0100;
    RegWrite = 1'b1;
    RegDst = 1'b0;
    Branch = 2'b00;
    MemRead = 1'b0;
    MemWrite = 1'b0;
    MemtoReg = 1'b0;
    ALUsrc = 1'b1;
    jump = 1'b0;
end

```

```

        6'h02: begin    //j
            ALUCtrl = 4'b0;
            RegWrite = 1'b0;
            RegDst = 1'b0;
            Branch = 2'b0;
            MemRead = 1'b0;
            MemWrite = 1'b0;
            MemtoReg = 1'b0;
            ALUsrc = 1'b0;
            jump = 1'b1;
        end

        default: begin    //andi default
            ALUCtrl = 4'b0000;
            RegWrite = 1'b1;
            RegDst = 1'b0;
            Branch = 2'b00;
            MemRead = 1'b0;
            MemWrite = 1'b0;
            MemtoReg = 1'b0;
            ALUsrc = 1'b1;
            jump = 1'b0;
        end
    endcase
end
end
endmodule

```

Instruction Memory:

```

module Instruction_Memory(
    input [31:0] Addr,
    output [31:0] Inst_out
);

    reg [7:0] imem[0:4095]; //2^12 byte addresses

    //Read Memory Contents, 2 bit offset for alignment
    assign Inst_out = {
        imem[{Addr[11:2],2'b0}+2'd3],
        imem[{Addr[11:2],2'b0}+2'd2],
        imem[{Addr[11:2],2'b0}+2'd1],
        imem[{Addr[11:2],2'b0}+2'd0]
    };

endmodule

```

Register Files:

```

module regfile32(
    input clk,
    input reset,
    input D_En,
    input [4:0] D_Addr,
    input [4:0] S_Addr,
    input [4:0] T_Addr,
    input [31:0] D,
    output wire [31:0] S,
    output wire [31:0] T
);

    //Instantiate 32 32-bit registers
    reg [31:0] regArray [0:31];

    //Assign S and T, specific contents of regArray
    assign S = regArray[S_Addr];
    assign T = regArray[T_Addr];

    //Write to regArray
    //regArray[0] inaccessible to overwriting
    always@(posedge clk, posedge reset) begin
        if(reset)
            regArray[0] <= 32'b0; else
            if(D_En && D_Addr)
                regArray[D_Addr] <= D;
    end
endmodule

```

First PC adder:

```

module PCADD(
    input [31:0] Din,
    output [31:0] PCADD_out
);

    assign PCADD_out = Din + 3'b100;
endmodule

```

Second PC adder:

```

module PCADD1(
    input [31:0] PCADDIn,
    input [31:0] SignEx,
    output [31:0] NextPC
);
    wire [31:0] SignSL;
    assign SignSL = SignEx << 2;
    assign NextPC = SignSL + PCADDIn;
endmodule

```

Branch:

```
module BranchSrc(  
    input [1:0] BranchIn,  
    input Zero,  
    output BranchOut  
);  
    wire notz, and1, and2;  
    not  
        notz(notz, Zero);  
  
    and  
        a1(and1, BranchIn[0], Zero),  
        a2(and2, BranchIn[1], notz);  
    or  
        ol(BranchOut, and1, and2);  
endmodule
```

PC Register:

```
module PC(  
    input clock,  
    input Reset,  
    input [31:0] Din,  
    output reg [31:0] PC_out  
);  
    always@(posedge clock, posedge Reset) begin  
        if(Reset)  
            PC_out <= 32'b0;  
        else  
            PC_out <= Din;  
        end  
    end  
endmodule
```

ALU:

```

module ALU(
    input [31:0] A,
    input [31:0] B,
    input [3:0] ALUctrl,
    output reg [31:0] ALUout,
    output reg N,
    output reg C,
    output Z,
    output reg V
);

assign Z = (ALUout == 0) ? 1'b1 : 1'b0;
reg signed [31:0] A_s, B_s;
always@(*) begin
    A_s = A; B_s = B;
    case(ALUctrl)
        4'b0000: begin //AND
            ALUout = A & B;
            C = 1'bx;
            V = 1'bx;
            N = ALUout[31];
        end
        4'b0001: begin //OR
            ALUout = A | B;
            C = 1'bx;
            V = 1'bx;
            N = ALUout[31];
        end
        4'b0011: begin //XOR
            ALUout = A ^ B;
            C = 1'bx;
            V = 1'bx;
            N = ALUout[31];
        end
        4'b0010: begin //Add Unsigned
            {C, ALUout} = A + B;
            V = C;
            N = 0;
        end
        4'b0110: begin //Subtract unsigned
            {C, ALUout} = A - B;
            V = C;
            N = 0;
        end
    end
end

```

```

4'b1100: begin //NOR
    ALUout = ~(A | B);
    C = 1'b0;
    V = 1'b0;
    N = ALUout[31];
end
4'b0111: begin //NOT
    ALUout = ~A;
    C = 1'b0;
    V = 1'b0;
    N = ALUout[31];
end
4'b1101: begin //SLL
    ALUout = A << 1;
    C = 1'b0;
    V = 1'b0;
    N = ALUout[31];
end
4'b1010: begin //add signed
    {C, ALUout} = A + B;
    if ((A[31] & B[31] & ~ALUout[31]) || (~A[31] & ~B[31] & ALUout[31]))
        V = 1'b1;
    else
        V = 1'b0;
    N = ALUout[31];
end
4'b1110: begin //subtract signed
    {C, ALUout} = A - B;
    if ((A[31] & ~B[31] & ~ALUout[31]) || (~A[31] & B[31] & ALUout[31]))
        V = 1'b1;
    else
        V = 1'b0;
    N = ALUout[31];
end
4'b0111: begin //SLL
    ALUout = A << 1;
    C = 1'b0;
    V = 1'b0;
    N = ALUout[31];
end

```

```

4'b1111: begin //SLT signed
    if ( A_s < B_s )
        ALUout = 32'b1;
    else
        ALUout = 32'b0;
        C = 1'bx;
        V = 1'bx;
        N = ALUout[31];
    end
4'b0100: begin //SLT unsigned
    if ( A < B )
        ALUout = 32'b1;
    else
        ALUout = 32'b0;
        C = 1'bx;
        V = 1'bx;
        N = ALUout[31];
    end
default: begin
    ALUout = 32'bx;
    {C, V, N} = 3'bxxx;
end
endcase
end
endmodule

```

Data Memory:

```

module DataMem(
    input clk,
    input mem_wr,
    input mem_rd,
    input [31:0] addr,
    input [31:0] wr_data,
    output [31:0] rd_data
);

    reg [7:0] dmem [0:4095];

    // write
    always@(posedge clk) begin
        if(mem_wr) begin
            dmem[addr[11:0] + 2'd3] <= wr_data[7:0];
            dmem[addr[11:0] + 2'd2] <= wr_data[15:8];
            dmem[addr[11:0] + 2'd1] <= wr_data[23:16];
            dmem[addr[11:0] + 2'd0] <= wr_data[31:24];
        end
    end

    //read
    assign rd_data = (mem_rd) ? { dmem[addr[11:0] + 2'd0],
                                   dmem[addr[11:0] + 2'd1],
                                   dmem[addr[11:0] + 2'd2],
                                   dmem[addr[11:0] + 2'd3] }
                                   : 32'hz;

endmodule

```

Sign Extension:

```

module SignExtension(
    input [15:0] SignExtIn,
    output [31:0] SignExtOut
);
    assign SignExtOut = {{16{SignExtIn[15]}}, SignExtIn};
endmodule

```

Results: (what we would do differently next time)


We feel like this time we really started early on the project and got a good feel for how the project worked. I noticed that for this project it was a lot easier to understand the diagram we were given and to translate it into Verilog. I think next time



I'm in a class learning a new language like Verilog
I'm going to watch some introduction videos on
Youtube.





Conclusion:

Adding functionality for the J-Type instruction has
taught us how interconnected the different R, I and
J-Type instructions are in a computer. It was
really cool to see how all the labs of the semester
came together in the end to form a final project
with R,I,and J-Type instructions.

RTL Schematic, Captured WaveForm:

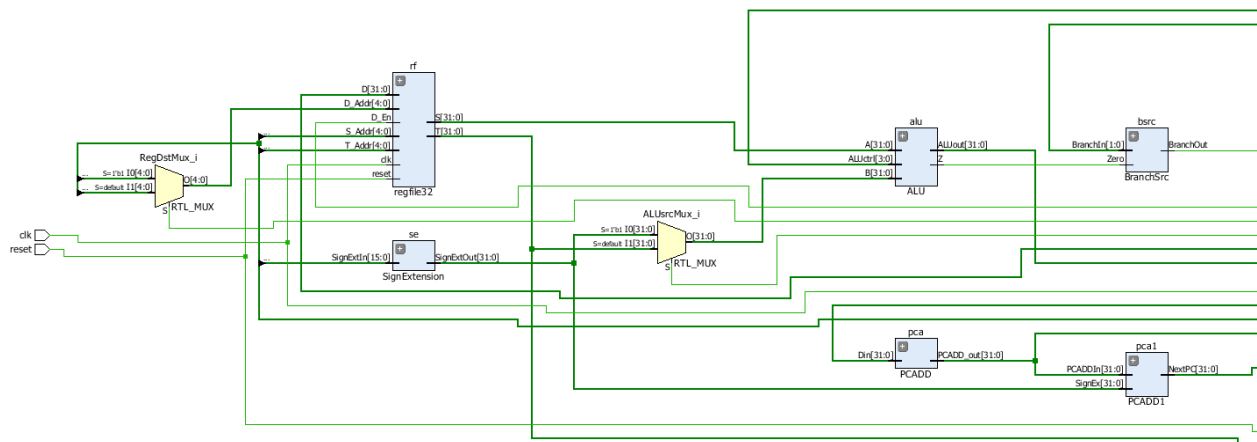

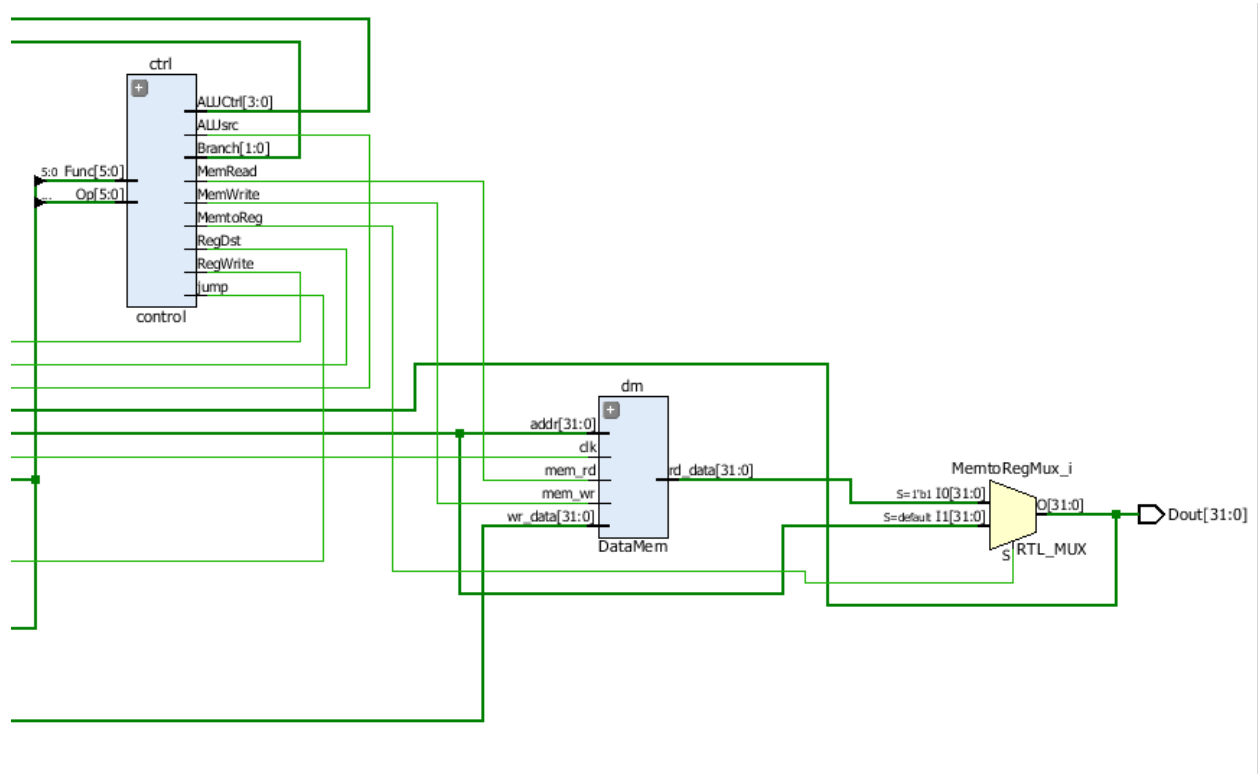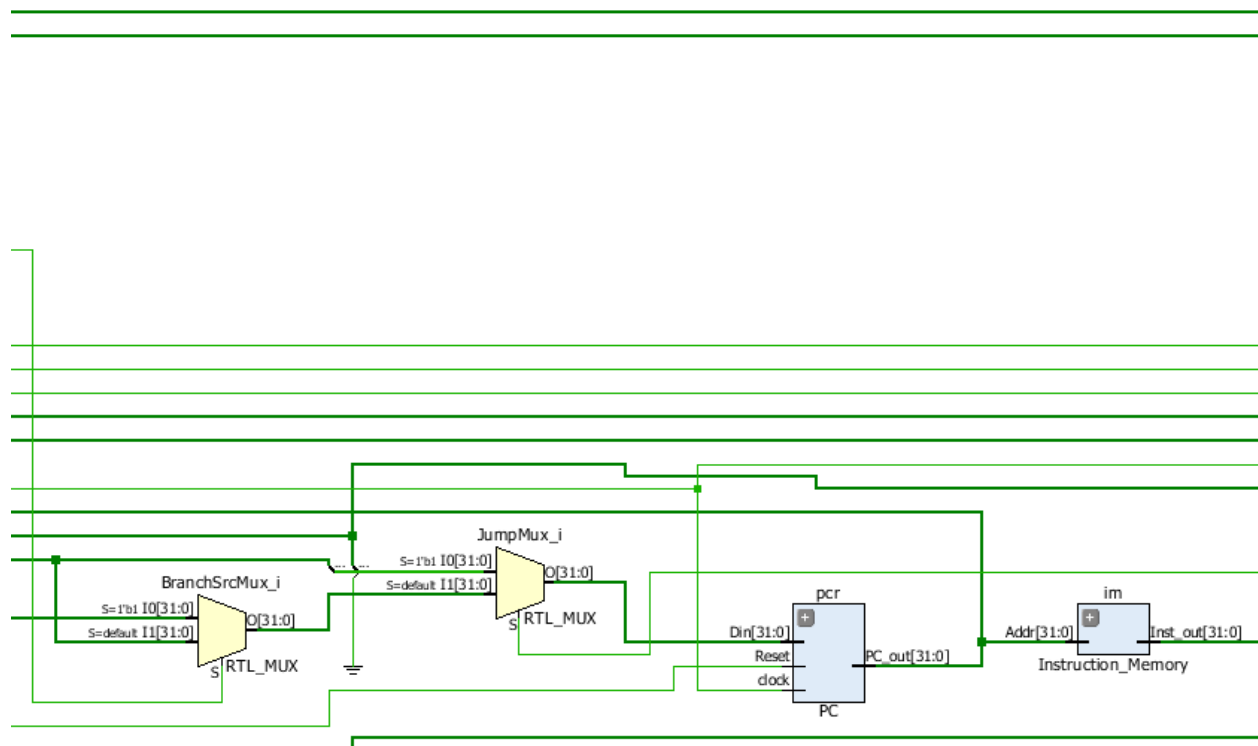

   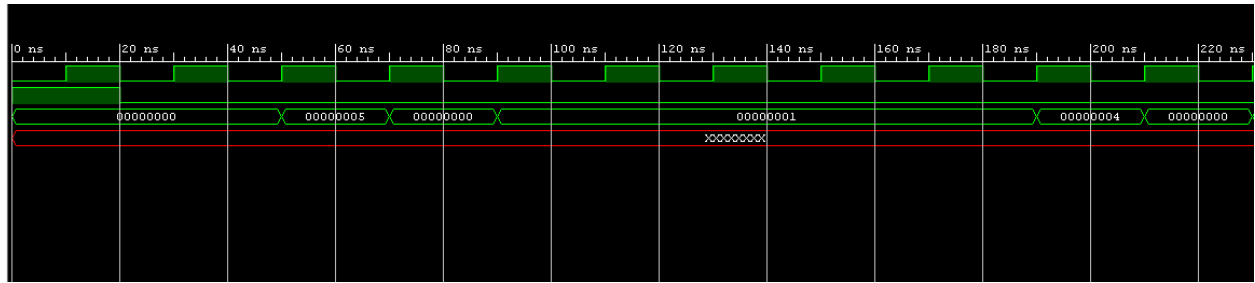

```
# run 1000ns
t= 930.0 ns dm[20]: 00000005
t= 950.0 ns dm[24]: 0000000f
t= 970.0 ns dm[28]: 00000005
t= 990.0 ns dm[32]: 00000014
$finish called at time : 990 ns
```